

■ General Description

There is a need to control the output voltage of a DC/DC converter from an external source.

In recent years, electronic products in most cases incorporate digital control, making use of a CPU.

This paper explains circuits incorporating a D/A converter that can be connected via a direct interface to a CPU.

A voltage-outputting D/A converter is used.


The FB version of a DC/DC converter is used. (The output voltage in the case of the FB version is set by external resistors.)

The circuits are usable for either step-down or step-up applications and at either FB voltage of 1 or 0.9 V.


■ Circuits

Example 1 (See figure below for component constants.)  
 Output voltage: 0.5 to 3.0 V  
 Resolution: 8 bits; 1 LSB: 10 mV  
 D/A converter full scale: 255  
 D/A converter output voltage: 0 to 2.5 V  
 D/A converter setting: 255 for output voltage of 0.5 V  
 D/A converter setting: 0 for output voltage of 3 V

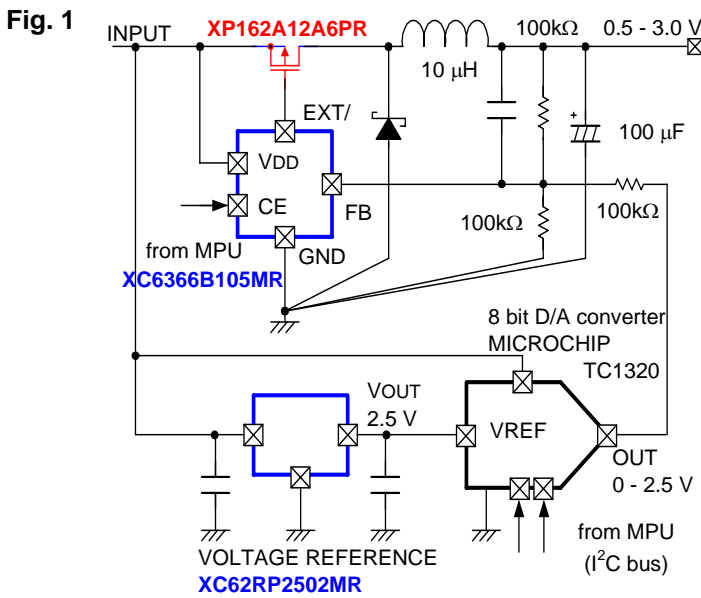Example 2 IC: XC9103/4/5 series Output voltage: 3 to 8 V  
 Resolution: 10 bits; 1 LSB: 5 mV, VREF voltage: 2 V  
 D/A converter full scale: 1024  
 D/A converter output voltage: 0 to 2 V  
 D/A converter setting: 1023 for output voltage of 3 V  
 D/A converter setting: 0 for output voltage of 8 V  
 RFB1=270 kΩ, RFB2=50 kΩ, RDAC=108 kΩ



■ Basic Circuit

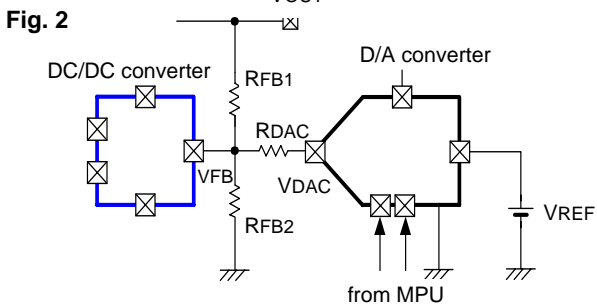

The output voltage of the D/A converter is passed through a resistor so that current is added at the FB pin to vary the output voltage of the DC/DC converter. A constant-voltage power supply is used as the reference voltage to the D/A converter.

■ Calculation

As a first step, choose an arbitrary value for RFB2.

$$\frac{1}{RFB2} = \left[ \frac{VOUTmax}{VFB} - 1 \right] \cdot \frac{1}{RDAC}$$

$$RDAC = \frac{VDAC \text{ variation}}{VOUT \text{ variation}} \times RFB1$$


$$VOUTmax = \left[ \frac{RFB1}{RFB2} + \frac{RFB1}{RDAC} + 1 \right] \times VFB$$

$$VOUTmin = \left[ \frac{RFB1}{RFB2} + 1 \right] \times VFB - \frac{RFB1}{RDAC} \times (VDACmax - VFB)$$

■ Principle of Operation

DC/DC converter output voltage: minimum  
 D/A converter output voltage: maximum

Fig. 3

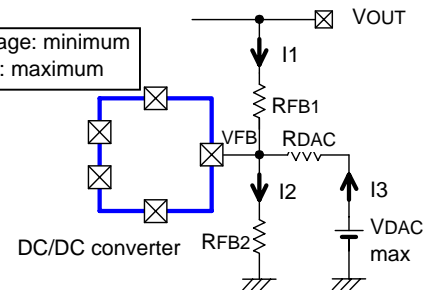


The output voltage, VOUT, decreases if current flows into the FB pin from the output voltage of the D/A converter, VDAC. The output voltage, VOUT, is inversely proportional to the output voltage of the D/A converter, VDAC.

$$I1 = I2 - I3, VOUT = I1 \cdot RFB1 + I2 \cdot RFB2$$

DC/DC converter output voltage: maximum  
 D/A converter output voltage: minimum (0)

Fig. 4

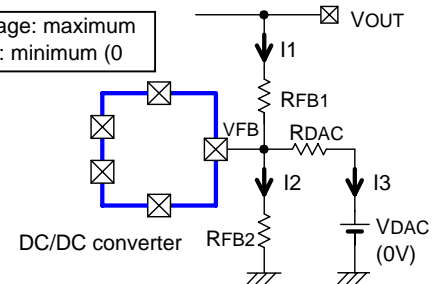

When the output voltage of the D/A converter, VDAC, is lower than the voltage at the FB pin, current flows from the FB pin to GND. When the output voltage of the D/A converter, VDAC, is zero, the output voltage becomes the maximum (VOUTmax).